

Name: \_\_\_\_\_ Department: \_\_\_\_\_ Student ID: \_\_\_\_\_

Team No.: \_\_\_\_\_ Date: \_\_\_\_\_ Lecturer's Signature: \_\_\_\_\_

**Introduction**

- (c) It is straightforward to derive the formula for the equivalent resistance for a parallel connection of  $N$  resistors  $R_i$ 's:

$$\frac{1}{R} = \sum_{i=1}^N \frac{1}{R_i}.$$

**Goals**

- Measure the capacitive time constant ( $\tau_{RC}$ ).
- Understand the capacitive reactance ( $X_C$ ).
- Understand the phase shift between current and voltage.

3. **Capacitance:** Consider a parallel plate capacitor of the cross sectional area  $A$  and distance  $d$ .

- (a) The capacitance is

$$C = \epsilon_0 \frac{A}{d},$$

where  $\epsilon_0$  is the permittivity constant for the vacuum.

- (b) It is straightforward to derive the formula for the equivalent capacitance for a parallel connection of  $N$  capacitors  $C_i$ 's:

$$C = \sum_{i=1}^N C_i.$$

- (c) It is straightforward to derive the formula for the equivalent resistance for a serial connection of  $N$  capacitors  $C_i$ 's:

$$\frac{1}{C} = \sum_{i=1}^N \frac{1}{C_i}.$$

**Theoretical Backgrounds****1. Potential Difference**

- (a) The potential difference  $V_R$  between the two terminals of a resistor of resistance  $R$  is

$$V_R = RI,$$

where  $I$  is the current,  $I = \frac{dq}{dt}$ .

- (b) The potential difference  $V_C$  between the two terminals of a capacitor of capacitance  $C$  charged with  $+q$  and  $-q$  is

$$V_C = \frac{q}{C}.$$

2. **Resistance:** Consider a resistor made of a uniform material of resistivity  $\rho$  with the cross sectional area  $A$  and length  $\ell$ .

- (a) The resistance is

$$R = \rho \frac{\ell}{A}.$$

- (b) It is straightforward to derive the formula for the equivalent resistance for a serial connection of  $N$  resistors  $R_i$ 's:

$$R = \sum_{i=1}^N R_i.$$

4. **Kirchhoff's Rule:** The algebraic sum of the changes in potential during a travel over a closed loop vanishes.

- (a) The formula is

$$\sum_{i=1}^N \Delta V_i = 0,$$

where  $i$  indicates each circuit element on that closed path.

- (b) The value is not vanishing if there is a changing magnetic field through the circuit that is not considered in this experiment.

5. **RC circuit with a square wave input**

- (a) This is the first-order linear differential equation:

$$v_R + v_C = R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E},$$

where  $\mathcal{E}$  is the potential difference between the two terminals of the battery.

- (b)
- Charging:**
- If
- $q(t=0) = 0$
- , then

$$\begin{aligned} v_C(t) &= \frac{q}{C} = \mathcal{E}(1 - e^{-t/\tau_{RC}}), \\ v_R(t) &= Ri = \mathcal{E}e^{-t/\tau_{RC}}, \end{aligned}$$

where  $\tau_{RC}$  is the **time constant**,

$$\tau_{RC} = RC.$$

- (c)
- Discharging:**
- If
- $q(t=0) = q_0 = CV_0$
- and
- $\mathcal{E} = 0$
- , then

$$\begin{aligned} v_C(t) &= \frac{q}{C} = V_0 e^{-t/\tau_{RC}}, \\ v_R(t) &= RI = -V_0 e^{-t/\tau_{RC}}. \end{aligned}$$

6. **RC circuit with a sine wave input**

- (a) This is the first-order linear differential equation with a sine wave input:

$$v_R + v_C = R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E}_m \sin \omega_d t,$$

where  $\omega_d$  ( $\mathcal{E}_m$ ) is the frequency (amplitude) of the sine wave input.

- (b) The current
- $i(t)$
- of the circuit is

$$i(t) = \frac{\mathcal{E}_m}{Z} \sin(\omega_d t - \phi),$$

where  $Z$  is

$$Z = \sqrt{R^2 + X_C^2},$$

$X_C$  is the **capacitive reactance**

$$X_C = \frac{1}{\omega_d C},$$

and  $\phi$  is the **phase constant**

$$\phi = \arctan\left(-\frac{X_C}{R}\right).$$

- (c) The potential difference
- $v_R(t)$
- of
- $R$
- is

$$\begin{aligned} v_R(t) &= i(t)R \\ &= \frac{\mathcal{E}_m R}{Z} \sin(\omega_d t - \phi). \end{aligned}$$

The phase of  $i(t)$  and that of  $v_R(t)$  are **in phase**.

- (d) The potential difference
- $v_C(t)$
- of
- $C$
- is


$$\begin{aligned} v_C(t) &= \frac{q(t)}{C} \\ &= \frac{1}{C} \int i(t) dt \\ &= -\frac{\mathcal{E}_m}{Z\omega_d C} \cos(\omega_d t - \phi) \\ &= \frac{\mathcal{E}_m}{Z\omega_d C} \sin(\omega_d t - \phi - \frac{\pi}{2}). \end{aligned}$$

The phase of  $i(t)$  **leads** that of  $v_C(t)$  by  $\frac{\pi}{2}$ , or the phase of  $v_C(t)$  **lags** that of  $i(t)$  by  $\frac{\pi}{2}$ .

- (e) The phase of
- $v_R(t)$
- leads**
- that of
- $v_C(t)$
- by
- $\frac{\pi}{2}$
- , or the phase of
- $v_C(t)$
- lags**
- that of
- $v_R(t)$
- by
- $\frac{\pi}{2}$
- .

**Instrumentation**

**1. Board RC**

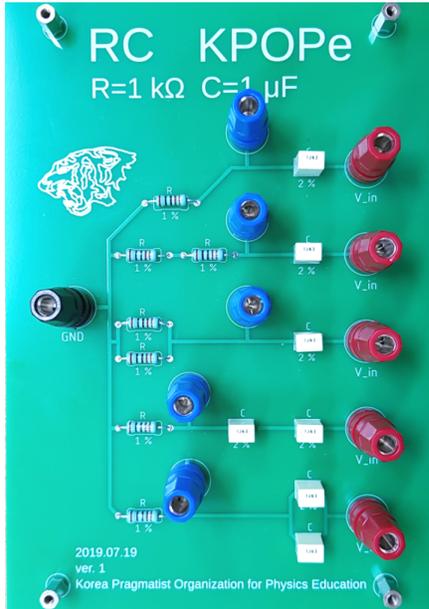

**2. Connection**



**Experimental Procedure**

**1. E1: a square wave input**

- (a) Carry out experiments with the five circuits on the board *RC*.
- (b) Connect the signal generator to  $V_{in}$  and the ground of the board.
- (c) Connect the voltage sensor across  $V_{in}$  and the ground.

- (d) Connect the voltage sensor across the resistor and the capacitor.
- (e) Set the waveform of the signal generator to **Positive Square Wave**.
- (f) Set the frequency and amplitude of the signal generator to 50 Hz and 1 V. Also check **Auto** of the signal generator.
- (g) Set the scope to watch each potential difference.
- (h) Set the trigger of the scope.
- (i) Select **Fast Monitor Mode** and click **Monitor** to observe.
- (j) Open the graph and plot the potential difference across the resistor and the capacitor.
- (k) Click **Highlight range of points in active data** and fit the data to

$$A + Be^{(-t/\tau)}$$

**2. E2: a sine wave input**

- (a) Carry out experiment with a circuit on the board *RC*.
- (b) Connect the signal generator to  $V_{in}$  and the ground of the board.
- (c) Connect the voltage sensor across  $V_{in}$  and the ground.
- (d) Connect the voltage sensor across the resistor and the capacitor.
- (e) Set the waveform of the signal generator to **Sine**.
- (f) Set the frequency and amplitude of the signal generator to 50 Hz and 1 V. Also check **Auto** of the signal generator.
- (g) Set the scope to watch each potential difference.
- (h) Set the trigger of the scope.
- (i) Select **Fast Monitor Mode** and click **Monitor** to observe.
- (j) Measure the phase difference between  $v_R$  and  $v_C$ .

## References

[1] **KPOP $\mathcal{E}$**  Digital Library: 

[2] **Y06:** *Capacitance* 

[3] **Y09:** *RC Circuit* 

[4] **Y16:** *Phase Shift in RLC Circuit* 